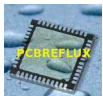





# Latch Circuit

## Requirements


- a switch can turn on the circuit (normally open or closed)
- the circuit should latch, i.e. stay on, until the ESP32 do its job
- the ESP32 should turn off the circuit
- the cuircuit should be battery powered
- should be able to switch more then 1A
- draw as low current as possible when off ( $<1\mu\text{A}$ )
- low voltage drop ( $<0,1\text{V}$ ), i.e. low  $R_{\text{dsOn}}$




# Latch Circuit

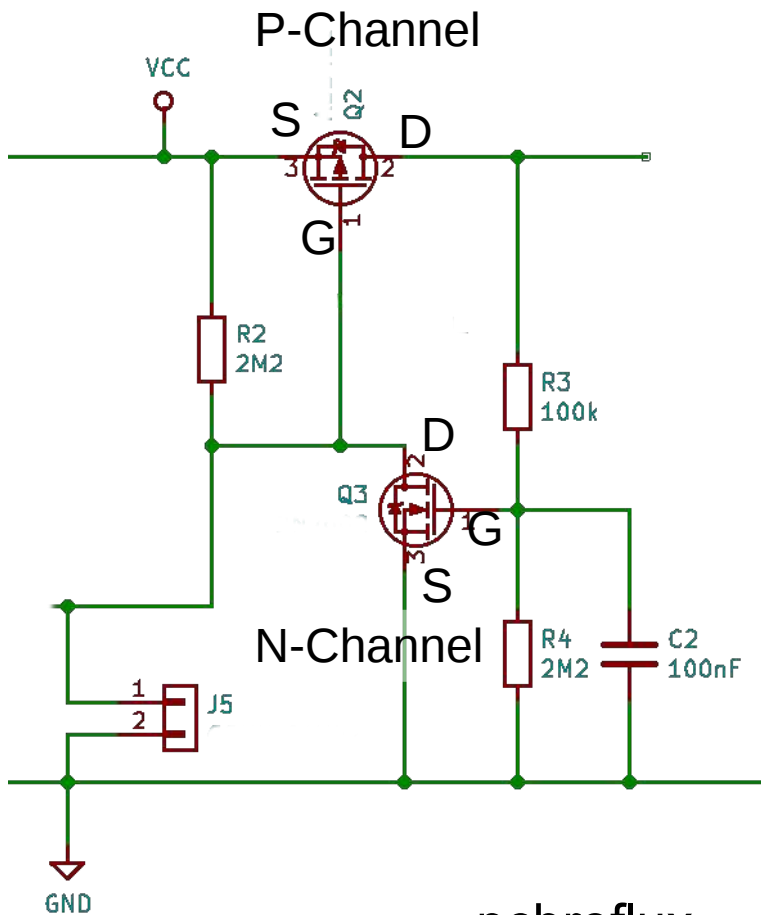


pcbreflux

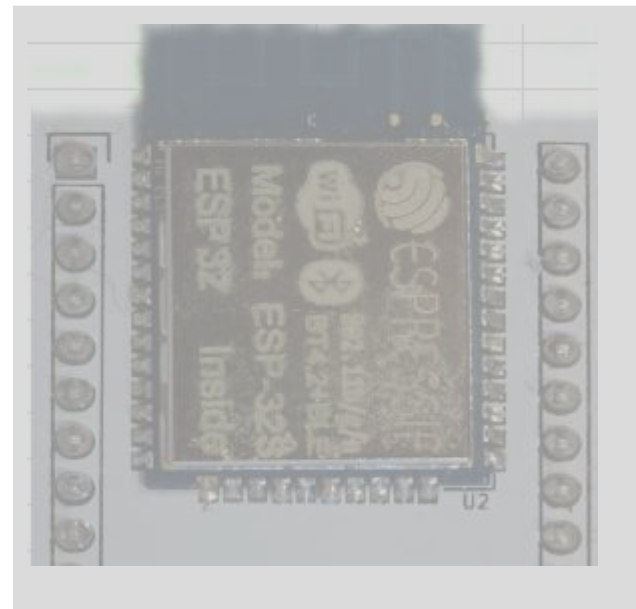


sample configuration

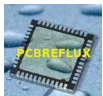


# Latch Circuit

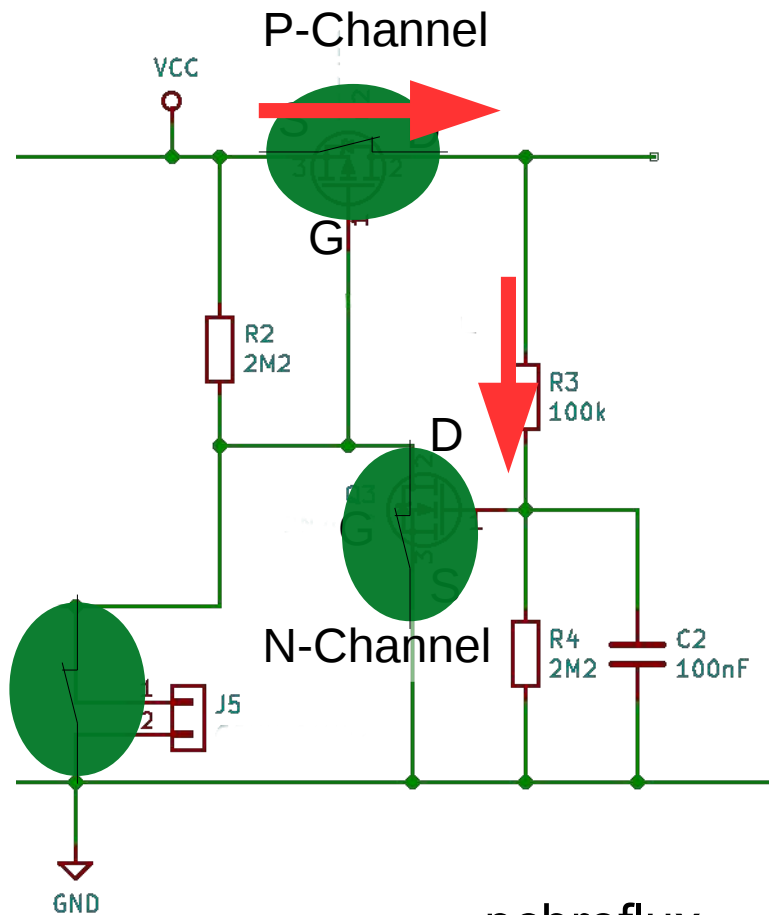


pcbreflux

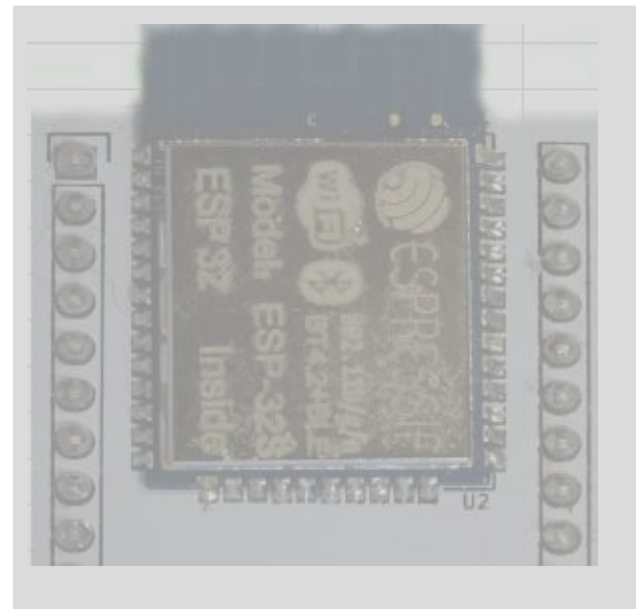


sample configuration

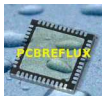


# Latch Circuit

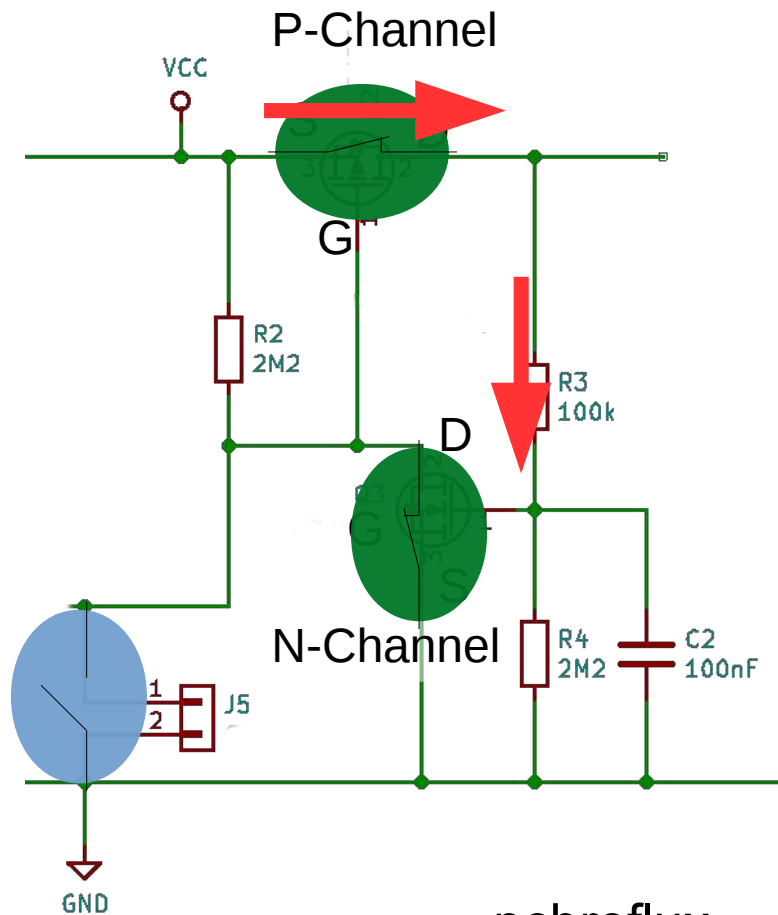


pcbreflux

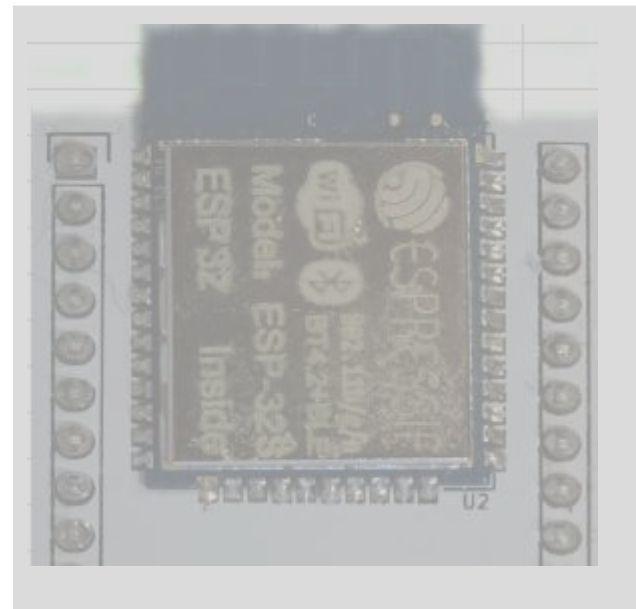


sample configuration


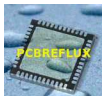


# Latch Circuit

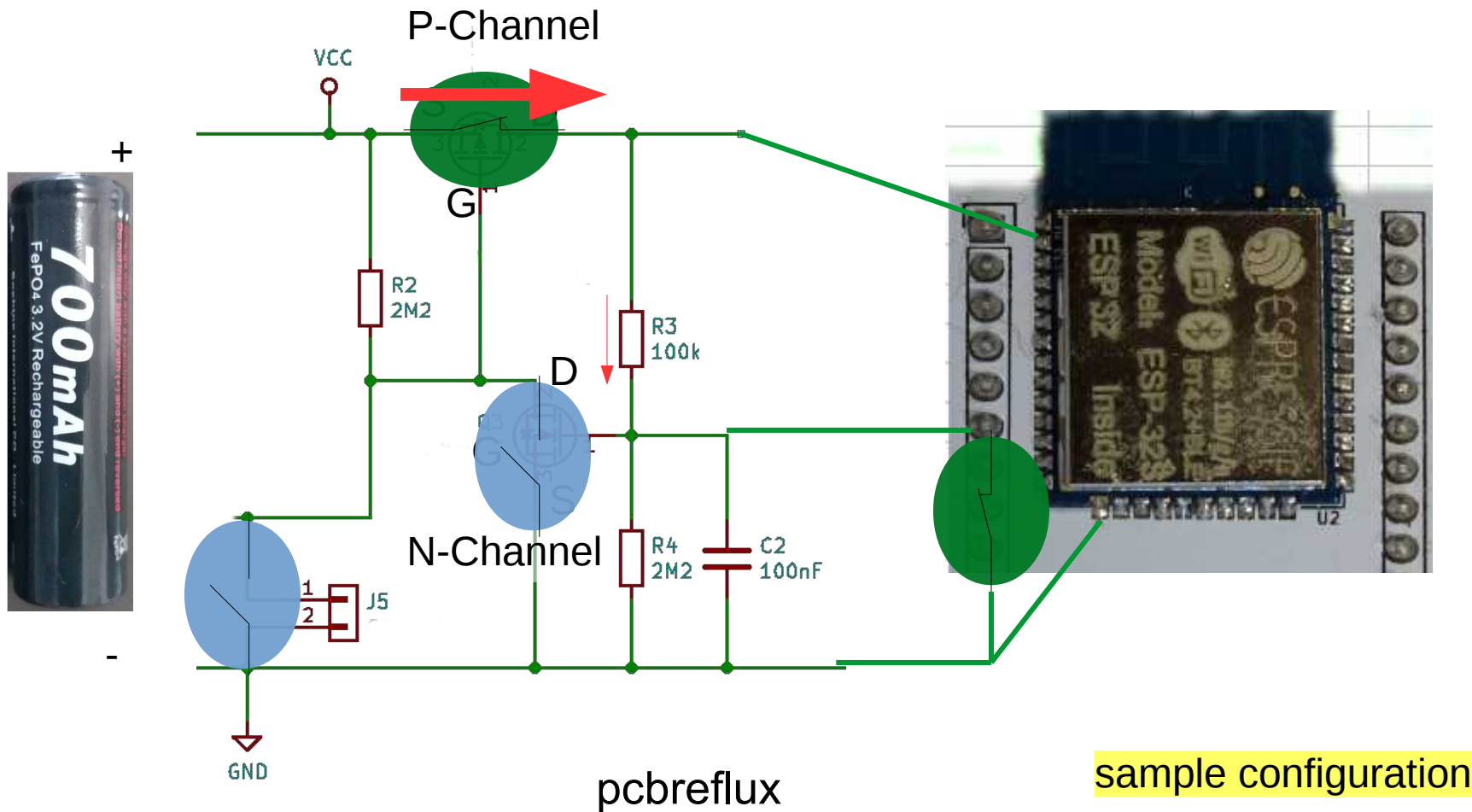

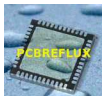

# Latch Circuit

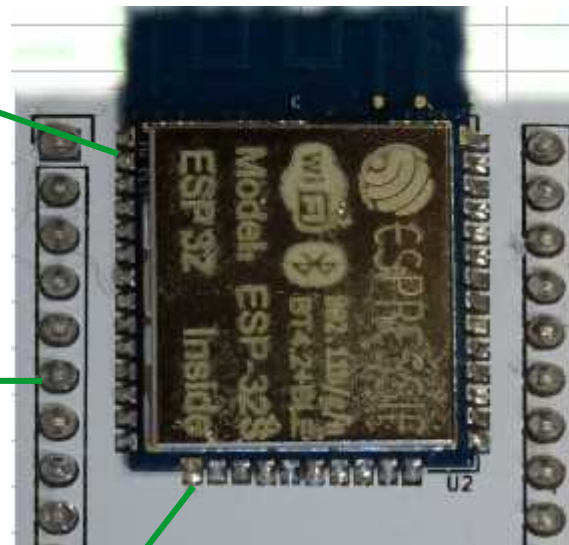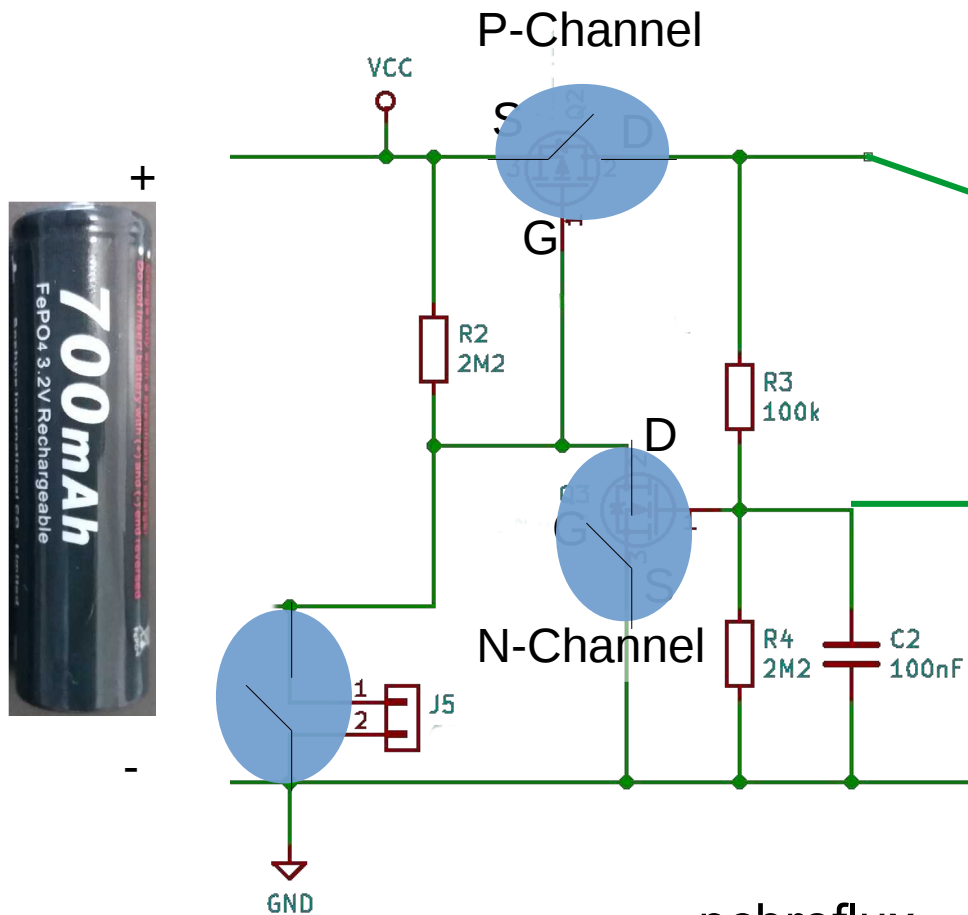

pcbreflux

sample configuration